

EXPERIMENT-1

CLASS-B POWER AMPLIFIER

(COMPLEMENTARY SYMMETRY AMPLIFIER)

- I. Aim:** a. To design class-B Complementary symmetry power amplifier with the observation of crossover distortion for small signal input.
b. To calculate the theoretical and practical values of max efficiency. $\{(\eta_{\max})_{\text{class-B}}=78\%\}$
- II. Specification:** The maximum efficiency required is 78% which need to be improved from class-A Power ampler. Take $V_{cc}=12V$, $V_{ss}=-12V$, use power transistors.
- III. Apparatus**
- Hardware:** a. Silicon-NPN-transistor 2N6517 Hardware-SL100
b. Silicon-PNP-transistor 2N6520
c. Resistors $R_L=470\Omega$
d. DRO
e. Signal generator
f. Bread board
- Software:** a. Circuit Simulator: to verify the functionality of NPN and PNP Transistors
b. NI-Multisim-14.0-desktop app: to calculate circuit parameters
- IV. Theory:**

About Transistors:

- I. BC107- BC stands for Buried Channel
- II. SL100 or CL100 –NPN (for Hardware)
- III. CK100 or SK 100- PNP (for Hardware)

About Power Amplifier:

Class-B Operation: In Class-B operation, each active element (transistor) conducts for only one-half (180 degrees) of the input signal cycle. Class-B amplifiers are more efficient than Class-A amplifiers but can introduce distortion, particularly crossover distortion, where there is a gap between the positive and negative halves of the signal. Complementary symmetry involves using both NPN (Negative-Positive-Negative) and PNP (Positive-Negative-Positive) transistors in the amplifier circuit. The NPN and PNP transistors work together to handle both positive and negative halves of the input signal, providing a balanced and symmetric operation. Combining these principles results in a Complementary Symmetry Class-B Power Amplifier, where both the positive and negative halves of the signal are handled by NPN and PNP transistors working in complementary pairs. This configuration aims to improve efficiency by allowing each type of transistor to handle the portion of the signal where it operates more efficiently.

- V. Schematic:** complementary symmetry circuit with distortion in class-B Power amplifier

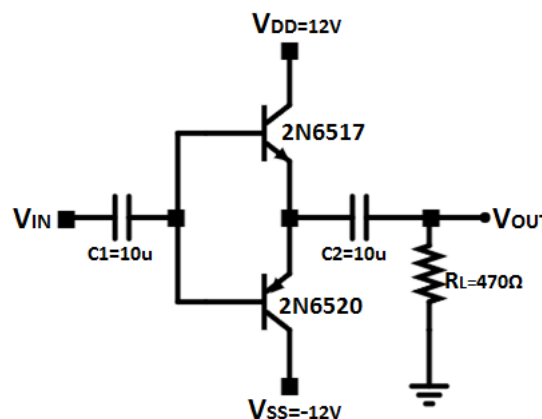


Figure 1. Zero bias complementary symmetry circuit

VI. Procedure:

- Connect the circuit as per the circuit diagram
- Apply 2 v p-p with 1KHZ frequency using function generator
- Observe the output in CRO.
- Note the cross over distortion in output.(output V_{p-p})
- Remove the collector connection and put ammeter.
- Note the I_{DC} value from VCC and VSS
- Using P_{DC} and P_{ac} formulas find the efficiency

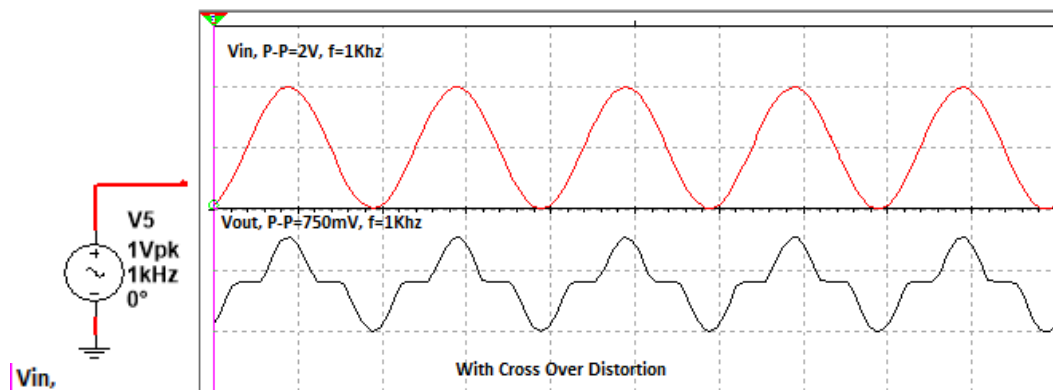
VII. Model graphs:

Figure 2. Input and output transient response of power amplifier, with crossover distortion

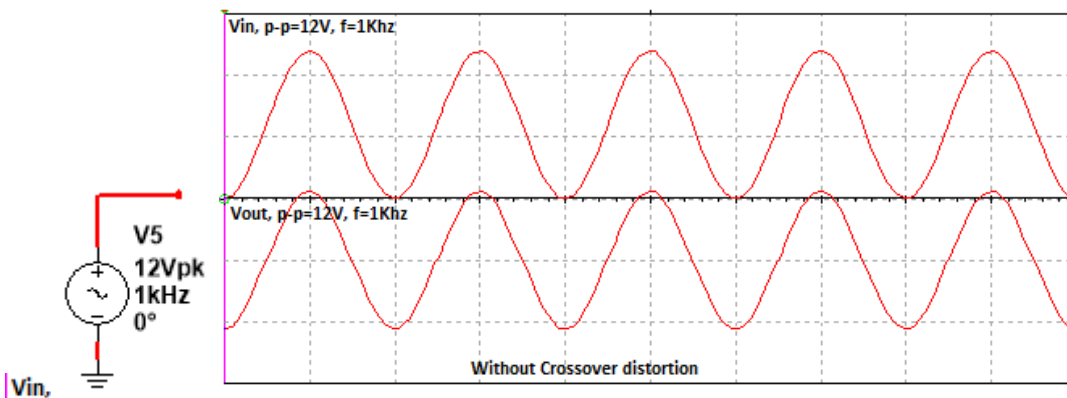


Figure 3. Input and output transient response of power amplifier, where crossover distortion is neglected due to large input

VIII. Observations:

- The AC input is applied to two transistors. During positive half cycle, NPN transistor conducts and PNP transistor does not conduct. During negative half cycle, PNP transistor conducts and NPN transistor does not conduct.
- To bring the transistor into active region from the cut off region, the transistor takes the cut in voltage from the input. Due to this, we get crossover distortion in class-B power amplifier which shown in figure 2.
- To make crossover distortion dominant the input strength is increased to the peak strength of V_{DD} so as to calculate maximum power dissipation as shown in the figure 3.

IX. Calculation of circuit Parameters

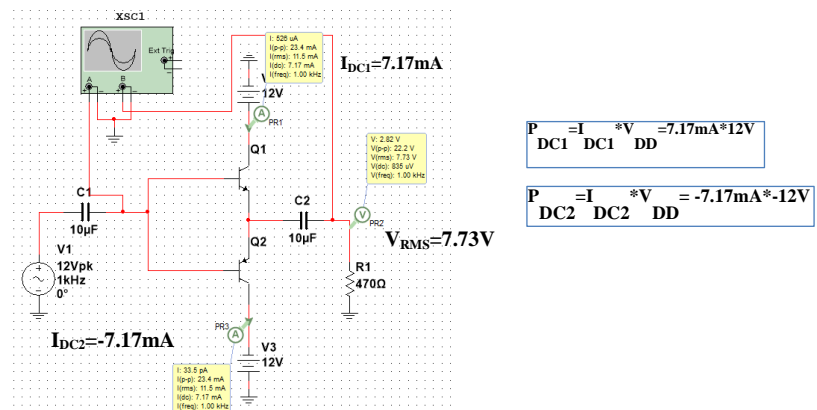


Figure 4. Calculations of I_{DC} from V_{CC} and V_{SS} branches to calculate DC input Power

Practical calculation of efficiency = $\% \eta_{MAX} = \frac{\text{Output AC power}}{\text{Input DC power}} = \frac{127.13\text{mW}}{172.08\text{mW}} = 73.8\%$

$$(\text{Input DC power})_{DC1} = V_{DD} \cdot \frac{I_m}{\pi} = 12 * I_{DC} = 12 * 7.17\text{mA} = 86.04\text{mW}$$

$$(\text{Input DC power})_{DC2} = -V_{DD} \cdot \frac{-I_m}{\pi} = -12 * I_{DC} = -12 * -7.17\text{mA} = 86.04\text{mW}$$

$$\text{Total DC Input Power} = P_{DC1} + P_{DC2} = 86.04\text{mW} + 86.04\text{mW} = 172.08\text{mW}$$

$$\text{Output AC power: AC power} = V_{rms} * I_{rms} = \frac{V_m}{\sqrt{2}} * \frac{I_m}{\sqrt{2}} = \frac{(V_{RMS})^2}{R_L} = \frac{(7.73)^2}{470} = 127.13\text{mW}$$

Theoretical calculation of efficiency = $\frac{\text{Output AC power}}{\text{Input DC power}}$

$$\% \eta_{MAX} = \frac{(V_{max} - V_{min})(I_{max} - I_{min})}{2 V_{CC} \cdot \frac{I_m}{\pi}} * 100 = \frac{\pi}{4} * 100 = 78.5\% \text{ (Where } (V_m)_{max} = V_{in-Peak} = V_{CC})$$


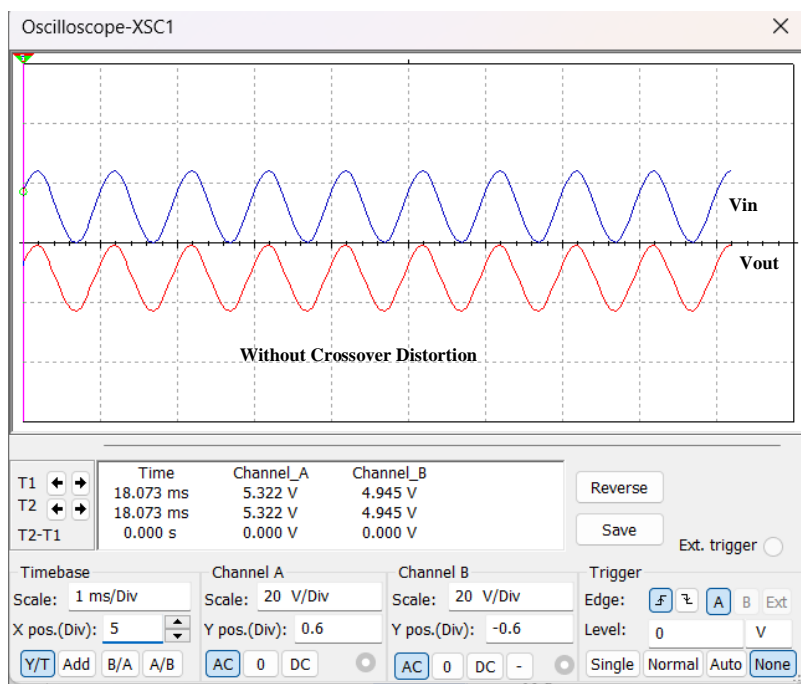


Figure 5. Input and output transient response of power amplifier, where crossover distortion is neglected due to large input

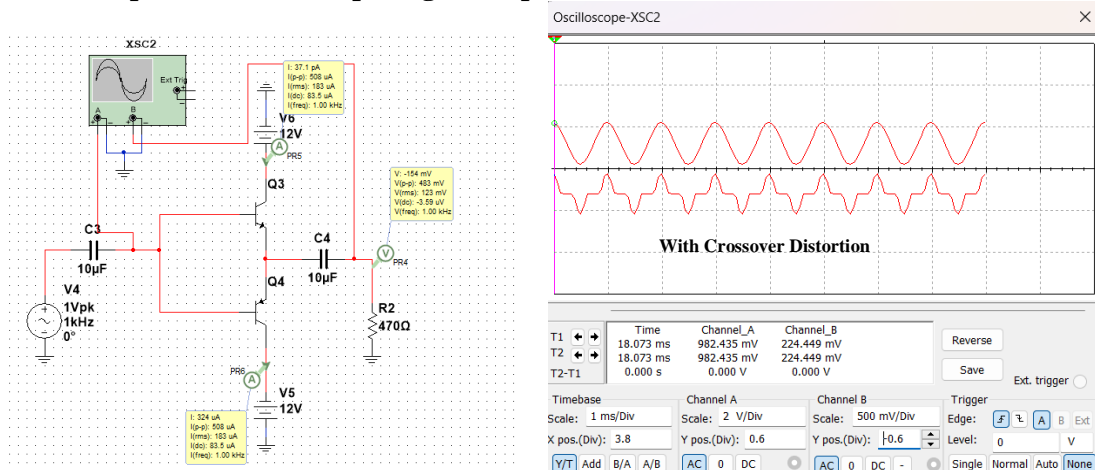X. Power amplifier with low input signal[1Vpk]:



Note:-If we give very low ac input signal, the transistor goes into the cut off region since transistor requires 0.7V to come out of the cut off region, so the signal gets distorted.

XI. Beyond the content : Modified as Class-AB Power Amplifier for eliminating distortion:


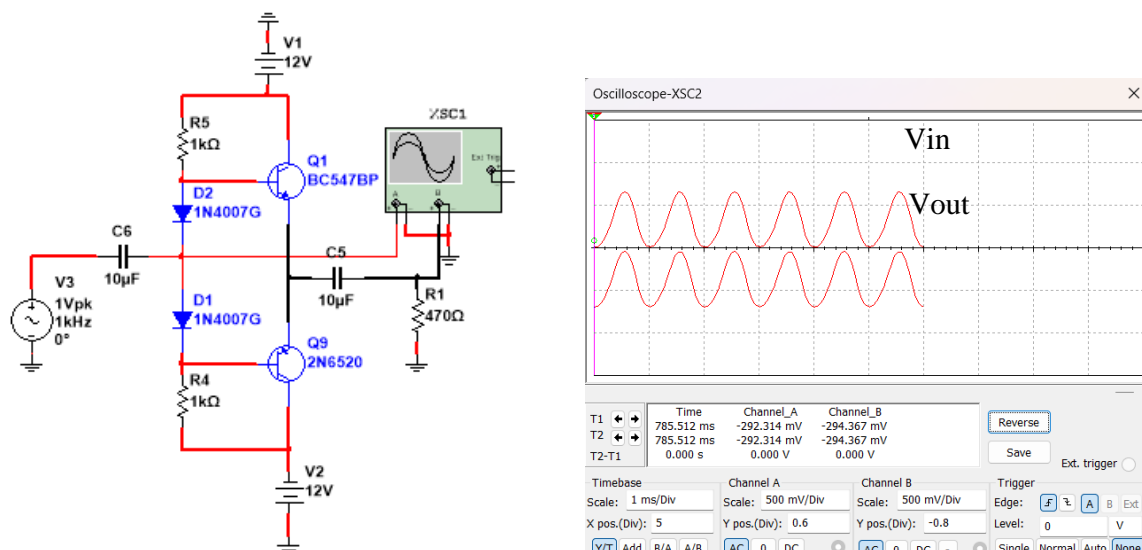


Figure 6. Class-AB power amplifier to eliminate the distortion for small signal input.

XII. Output for RL=1MΩ:

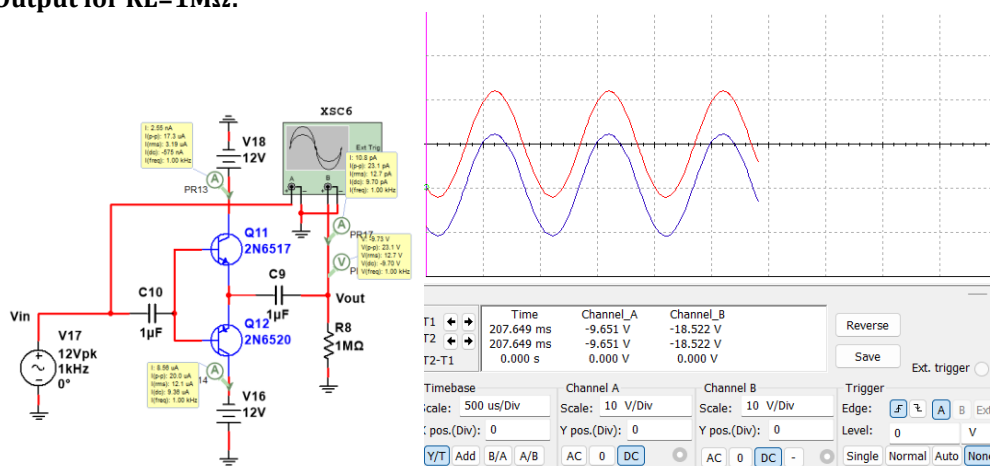

As RL increases the O/P Wave form is shifting downwards and I/P and O/P are in phase and vice-versa.

XIII. Result:

Efficiency(η)	
Theoretical	78.5%
Practical	73.8%

Signature of the Faculty